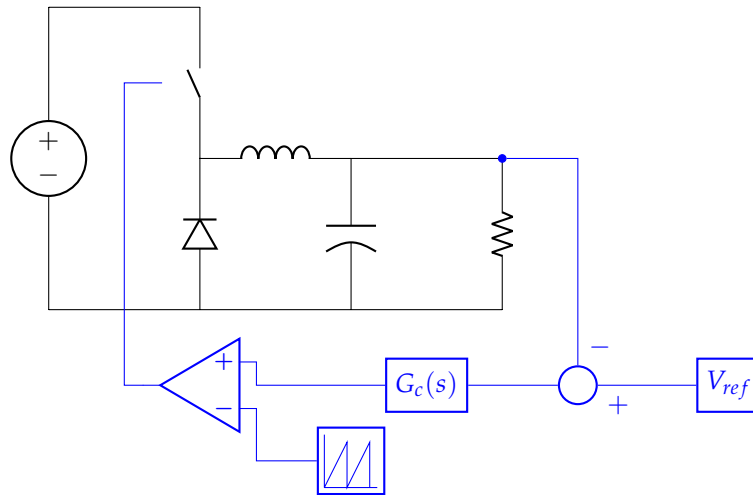


DIGITAL CONTROL OF POWER ELECTRONICS

Voltage Mode Control of Buck Converter




The plant for a buck converter in continuous conduction mode is shown below.

$$\frac{v_o}{d} = \frac{V_{in}}{LC} \frac{1 + srC}{s^2 + s \left(\frac{1}{RC} + \frac{r}{L} \right) + \frac{1}{LC}} \quad (1)$$

The parameters of the buck converter are shown below.

$$V_{in} = 30, V_o = 15, L = 200\mu H, C = 400\mu F, r = 0.1, R = 5 \quad (2)$$

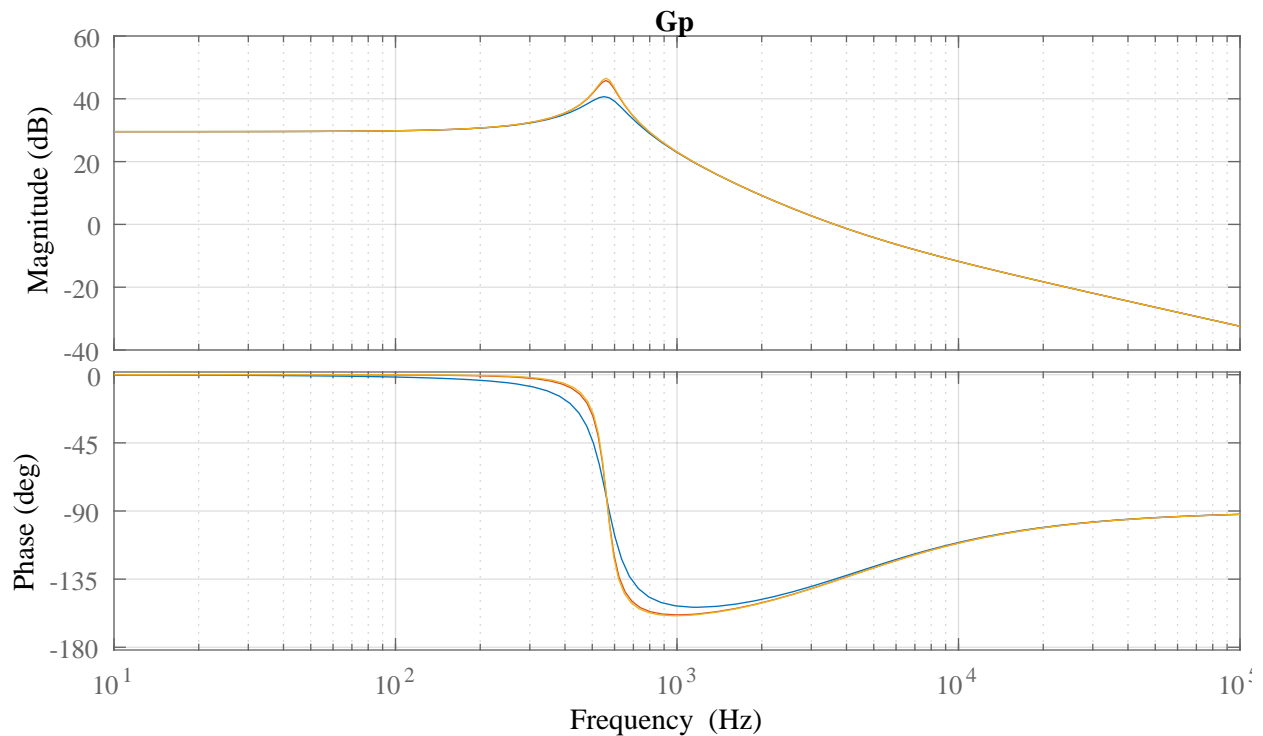Note, the plant has a complex pole pair and one zero.



Design the controller below, find the zero, pole and gain for a bandwidth of $f_c = 5\text{kHz}$ and phase margin of 60 degrees.

$$G_c(s) = \frac{k \left(1 + \frac{s}{\omega_z}\right)^2}{s \left(1 + \frac{s}{\omega_p}\right)^2} \quad (3)$$

Evaluate the gain of phase of the plant at the desired bandwidth

$$|G_P(s)|_{s=j\omega} \quad (4)$$

$$\angle G_P(s)|_{s=j\omega} \quad (5)$$

$$\phi_{boost} = -90^\circ + \phi_{PM} - \angle G_{PS}(s)|_{s=j\omega} \quad (6)$$

$$k_{boost} = \tan\left(45^\circ + \frac{\phi_{boost}}{4}\right) \quad (7)$$

$$k = \frac{1}{|G_{PS}(s)|_{s=j\omega}} \quad (8)$$

$$\omega_z = \frac{2\pi f_c}{k_{boost}} \quad (9)$$

$$\omega_p = 2\pi f_c k_{boost} \quad (10)$$

```

1 clear
2
3 s=tf('s')
4 opts = bodeoptions('cstprefs');
5 opts.FreqUnits = 'Hz';
6 Vin = 30
7 L = 200e-6
8 C = 400e-6
9 r = 0.1
10 R = 5
11 Gps = Vin/(L*C) * (1+s*C*r) / (s^2 + s*(r/L + 1/(R*C)) + 1/(L *C) )
12
13 fc = 5e3 % select bandwidth
14 pm = 60 % select phase margin
15 kfb = 1 % gain in feedback voltage measurement
16 Gpwm = 1 % gain of the modulator
17
18 [gain phase] = bode(Gps,2*pi*fc)
19 phiboost = -90 + pm - phase
20 kboost = tand(45 + phiboost/4)
21 gaincontroller = 1 / (kfb * Gpwm * gain)
22 fz = fc/kboost
23 fp = fc*kboost
24 kc = gaincontroller * 2*pi*fz/kboost
25 wz = 2*pi*fz
26 wp = 2*pi*fp

```

$$\omega_z = 11954 \quad \omega_p = 82556 \quad k = 7364 \quad (11)$$

